




Current

What is Current?

Current is the **flow of electrons** through a circuit.


Why do Electrons Move?

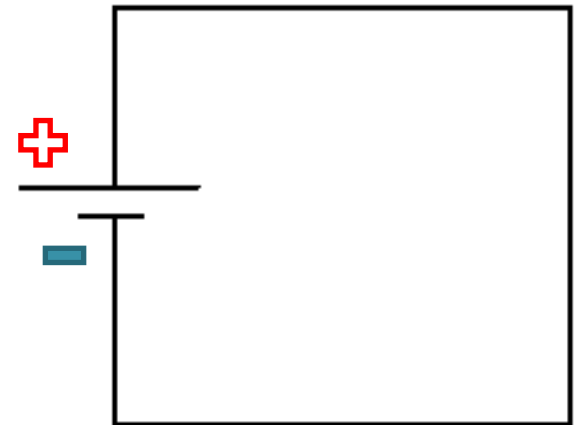- An electrochemical cell (battery) uses chemical reactions to move electrons. This creates a “potential difference” between the ends of the battery.
 - Positive terminal is positively charged
 - Negative terminal is negatively charged and has an excess of **electrons**




Why do Electrons Move?

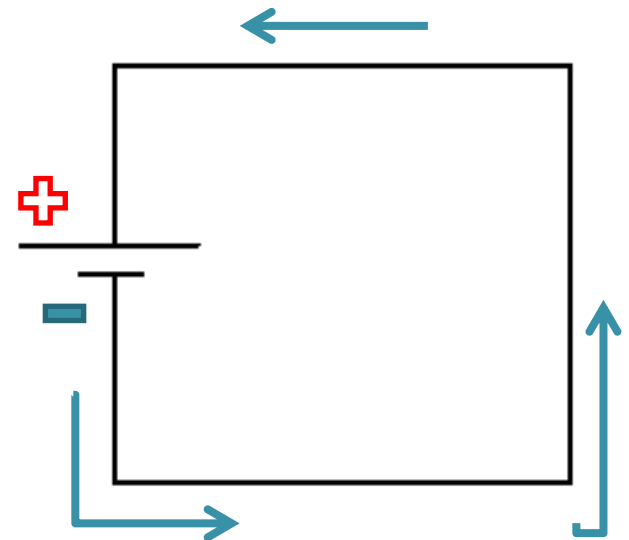- When a circuit connects the two ends of the cell, current flows through the wire.
 - Electrons are repelled by the **negative** terminal and are attracted by the **positive** terminal.
 - Electrons cannot move through **air (insulator)** but they can definitely move through a **wire (conductor)**!




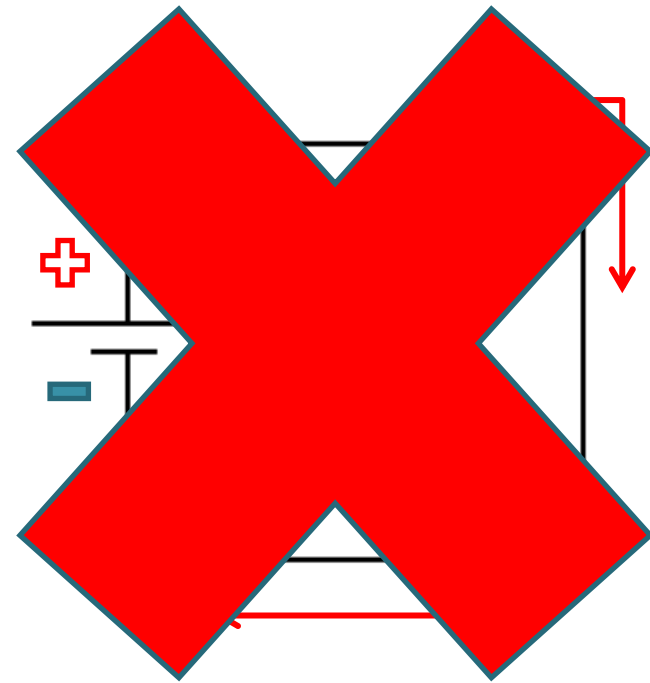- When scientists discovered electric current, they assumed that positive charges were moving.
- This is called **conventional current**
 - defined as the direction positive charges move in a circuit
 - from positive to negative
 - we now know this isn't the way it actually works.



Calculating Current

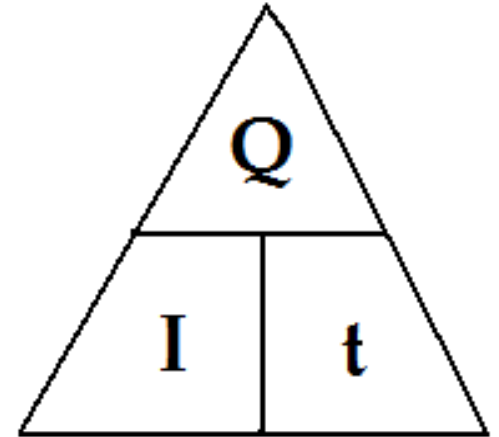
Current is the amount of charge that passes a point in a circuit every second:



$$I = \frac{Q}{t}$$


- I**: is the symbol for **current**, measured in **amperes (A)**
- Q**: is the symbol for **charge**, measured in **coulombs (C)**
- t**: is **time**, measured in **seconds (s)**

Example #1

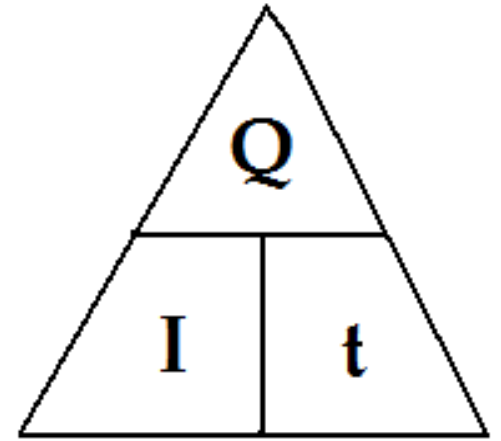

What is the current in a wire if 25 C of charge passes by a point in 5 seconds?
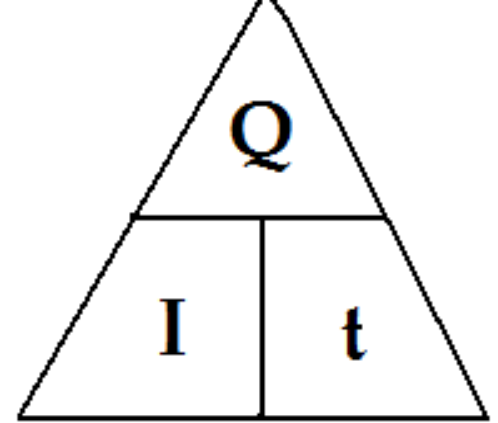
$$I = \frac{Q}{t} = \frac{25C}{5s} = 5A$$



Example #2

If the current in a wire is measured to be 12 A, how much charge passes by a point in the circuit every minute?

$$\begin{aligned} Q &= I \times t \\ &= 12A \times 60s \\ &= 720C \end{aligned}$$

Example #3

A current of 64 mA is equivalent to _____ A.

$$64 \text{ mA} \times \frac{1\text{A}}{1000\text{mA}} = \boxed{0.064 \text{ A}}$$

Example #4


A current of 0.0028 A is equivalent to _____ mA.

$$64 \text{ mA} \times \frac{1\text{A}}{1000\text{mA}} = \boxed{0.064 \text{ A}}$$

- Current is measured by a device called an **ammeter**.



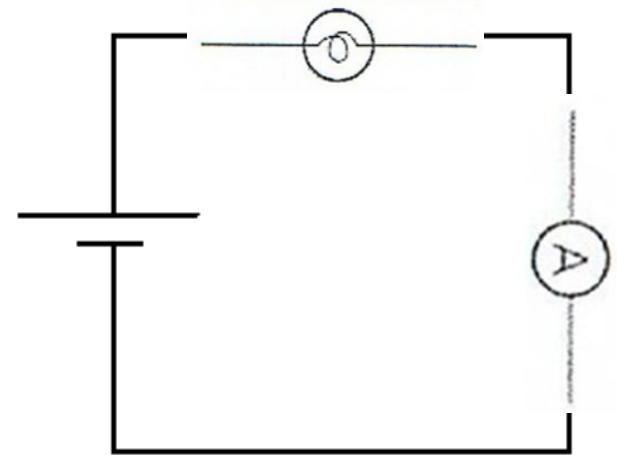- Typical amounts of current:
 - In a light bulb is 1A
 - In a TV is 4A
 - In a car starter is 500 A




Series vs. Parallel

In a circuit, devices (such as light bulbs or batteries) can be placed in two different ways.

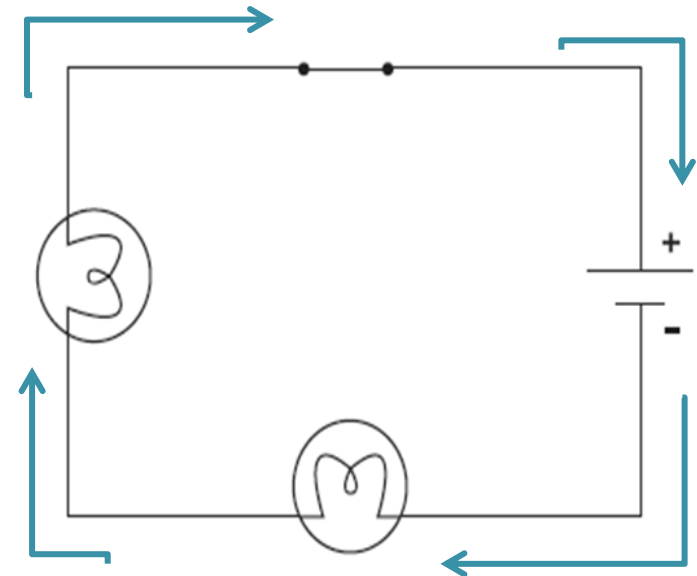
I. SERIES

- When devices are placed in series, the current goes through a **single path** through all devices.
- In this circuit, there is only **one path** and the **current** goes through the two light bulbs in the **series**.



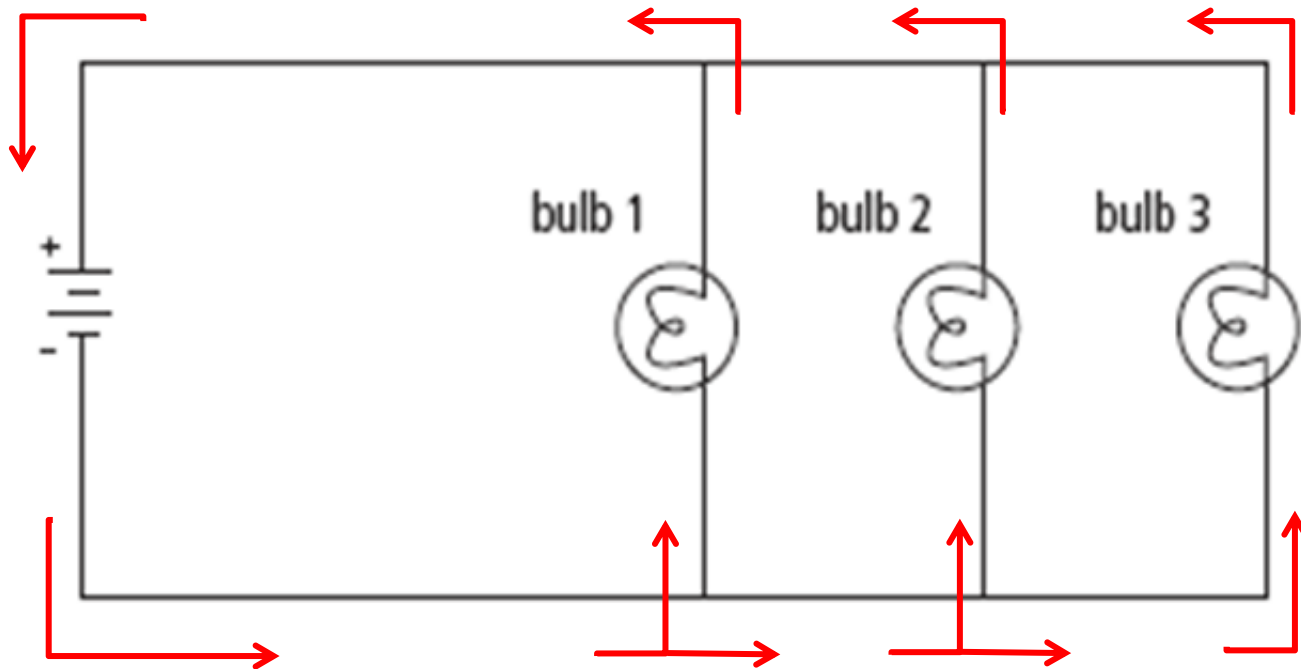2. PARALLEL

- When devices are placed in parallel, there are 2 or **more paths** that the **current** can take
- Current **splits**: some electrons go through one device, and some go through the other(s).




- Decide whether each circuit is Series, Parallel, or a Combination of the two.


A.




B.

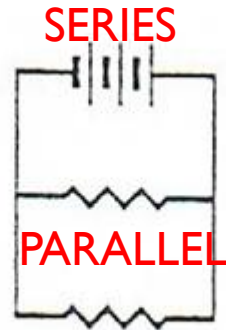


C.

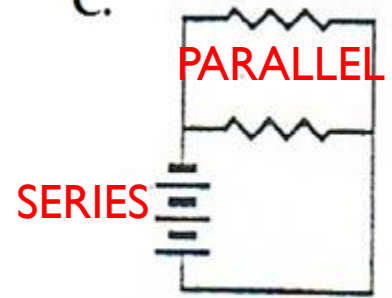


D.

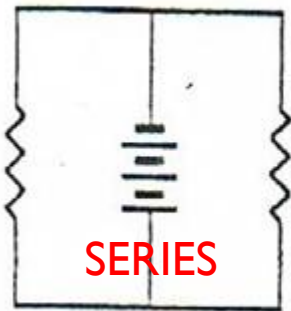

E.

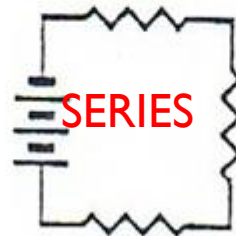


F.

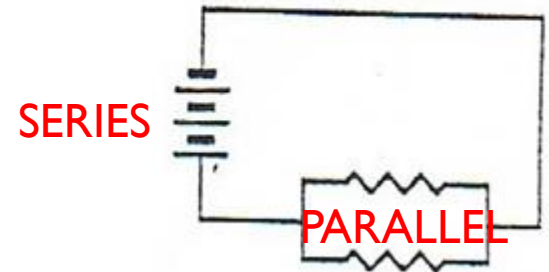


Calculating Current in SERIES

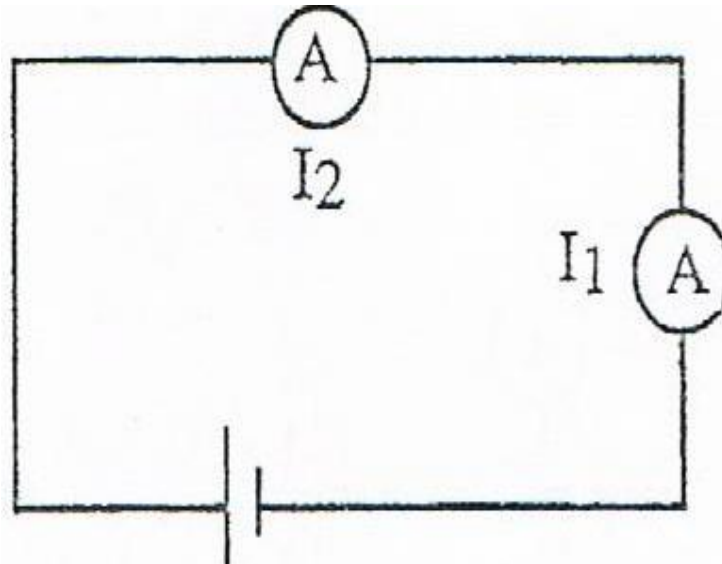- **Current (I)**
 - Measured in Amperes (A)
 - When you place an Ammeter in SERIES the current **stays the same**
- Series: $I_{Total} = I_1 = I_2$




Calculating Current in PARALLEL

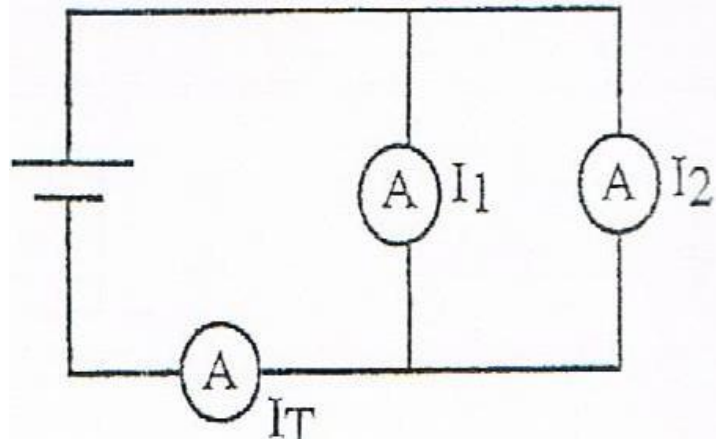- **Current (I)**
 - Measured in Amperes (A)
 - When you place an Ammeter in PARALLEL, you **add** the current to find a total.
- Parallel: $I_{Total} = I_1 + I_2 + \dots$



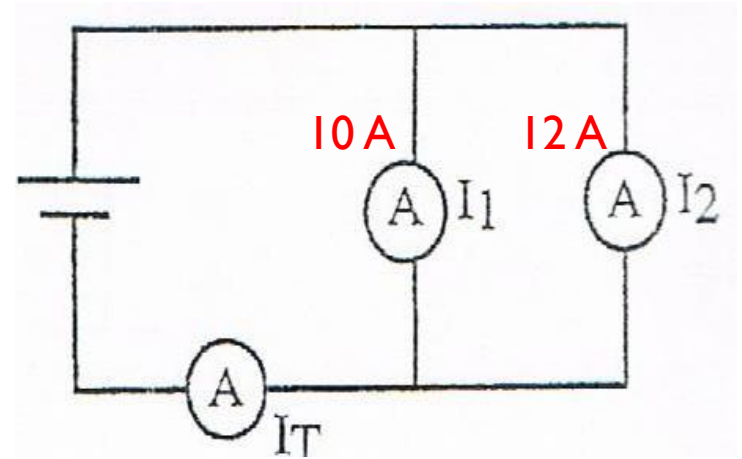Example #4

Find the total current for the following circuit.




$$I_{Total} = I_1 + I_2$$

$$= 10\text{ A} + 12\text{ A}$$

$$= \boxed{22\text{ A}}$$

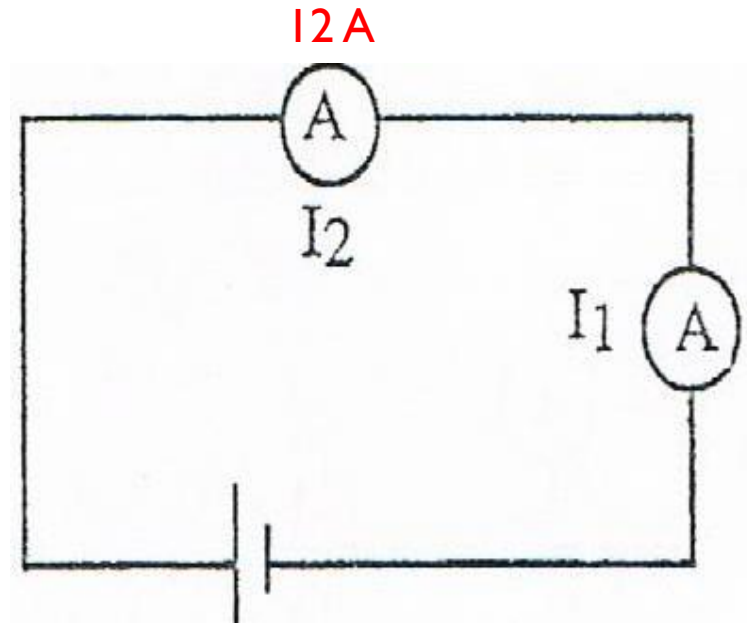Example #5


Find the total current for the following circuit.



$$I_{Total} = I_2 = I_1 = 12A$$

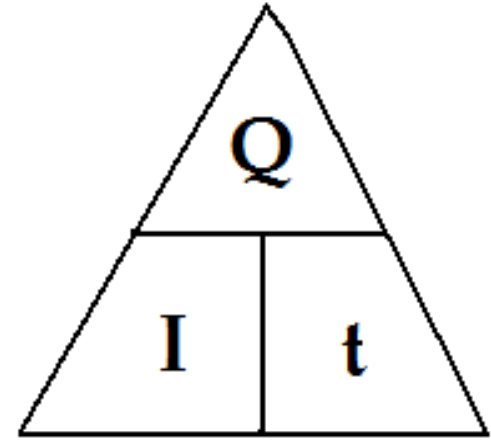Example #6

How long does it take 40 C of charge to pass by a point if the current in the circuit is 0.76 A ?



$$t = \frac{Q}{I} = \frac{40C}{0.76A} = 52.6s$$