

Ohm's Law

- The relationship between **voltage, current and resistance** is given by Ohm's Law:

$$\mathbf{V = IR}$$

$$\mathbf{Voltage (V) = Current (I) \times Resistance (R)}$$

Volts (V) amps (A) ohms (Ω)


- The greater the resistance, the lower the current.
- The lower the resistance, the higher the current.

Ohm's Law

You can rearrange the formula to calculate resistance and current:

$$\text{resistance} = \text{voltage} \div \text{current} \quad \text{or} \quad R = \frac{V}{I}$$

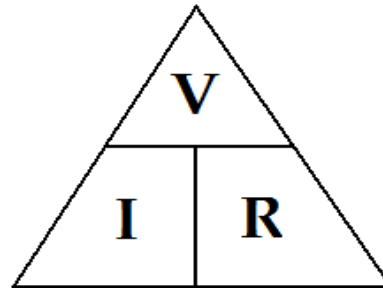
$$\text{current} = \text{voltage} \div \text{resistance} \quad \text{or} \quad I = \frac{V}{R}$$



Fill in the following table and calculate Resistance.

Voltage (V)	Current (A)	Resistance (Ω)
3.0	1.2	2.4 Ω
4.5	1.7	2.65 Ω
6.0	2.5	2.4 Ω
9.0	3.6	2.5 Ω
12.0	5.0	2.4 Ω

Example #1

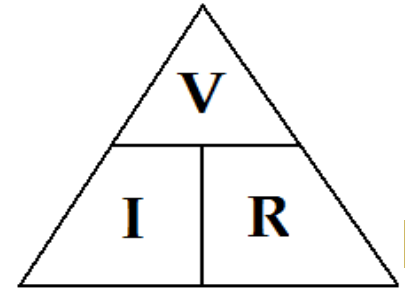


A current of 2.5 mA flows through a resistor when connected to a 16 V power supply.

What is the value of this resistor?

$$\begin{aligned} R &= \frac{V}{I} \\ &= \frac{16 \text{ V}}{0.0025 \text{ A}} \\ &= \boxed{6400 \ \Omega} \end{aligned}$$

Example #2

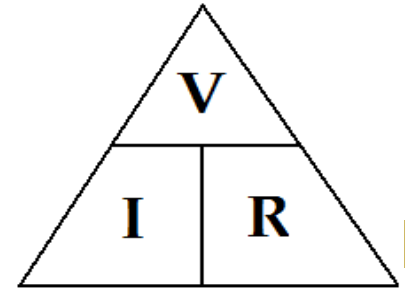

What is the current produced by a potential difference of 240 volts through a resistance of 0.2 ohms?

$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{240 \text{ V}}{0.2 \Omega} \\ &= 1200 \text{ A} \end{aligned}$$