


Series and Parallel Circuits Lab

Purpose:

- Describe the relationship in between, potential difference, current and resistance for series and parallel circuits


Instructions:

- Go to “Phet - Circuit Construction Kit: DC” simulation from https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc_en.html and select “Lab”
- Play around and try to learn how to use the simulation (how to connect, disconnect, change values of a circuit element, how to use voltmeter and ammeters) for 5 minutes.

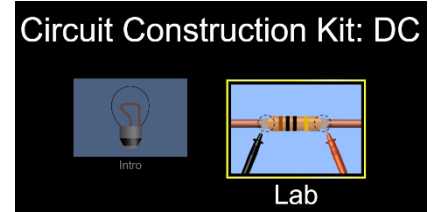

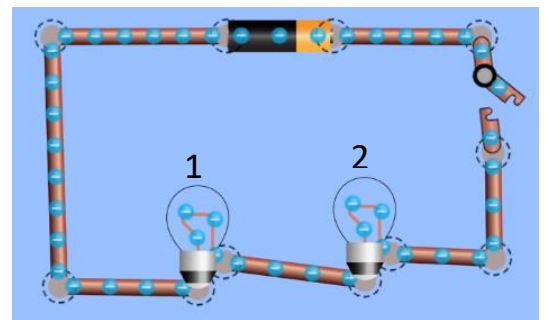Part 1: Series Circuits

- Construct the circuit on the right.
- Set the voltage to 60V and resistance of the lightbulbs to 10 ohms.




1. *Predict: What potential difference will you find across the first lightbulb? The second lightbulb?*

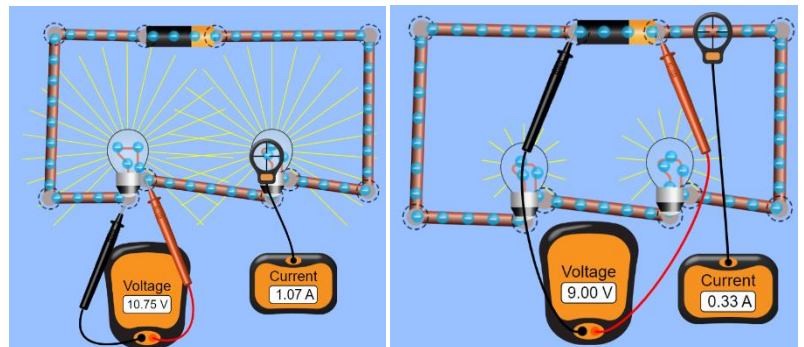2. *Predict: What current will you find through the first lightbulb? The second lightbulb?*

- Use the voltmeter and ammeter to measure the voltage and current across each light bulb. Record your results on Table 1.
- Next add one more lightbulb (#3) with **10 ohms** of resistance in **series** to the circuit. Measure the voltage and current across each light bulb. Record your results in Table 1.
- Lastly, add one more lightbulb (#4) with **30 ohms** of resistance in series and record the measurements.

- ❖ To measure potential difference across the lightbulb, place the black probe to one end and place the red probe to the other end of the lightbulb.
- ❖ To measure the current through a lightbulb, place the center of the circular probe on the wire inside the lightbulb.
- ❖ To measure total potential difference across the circuit, place the black probe to one end and place the red probe to the other end of the battery.
- ❖ To measure the total current through the circuit, place the center of the circular probe on the wire right after the battery.



7. How does the speed of electron movement change when more lightbulbs are added in parallel?
8. How does lightbulb brightness change when more lightbulbs are added in parallel?
9. What is the relationship between the total current of the circuit and individual lightbulb currents in parallel?
10. What is the relationship between the total voltage of the circuit and individual lightbulb voltages in parallel?
11. How do you suppose electrical appliances are connected in our houses? In parallel or in series? Why?(Hint: What happens to other appliances when one appliance is turned off?)
12. A student is recording the following measurements on the table. **Fill in the rest of the table** and construct a circuit that is going to be aligned with the numbers on the table below. Then **draw that circuit** below.

V_{tot} (V)	I_{tot} (A)	R_1 (Ω)	V_1 (V)	I_1 (A)	R_2 (Ω)	V_2 (V)	I_2 (A)
	3 A		12 V	1 A		12 V	